

1. A parallel-plate capacitor is constructed by filling the space between two square plates with blocks of three dielectric materials, as in Figure 1. You may assume that $l \gg d$. Find an expression for the capacitance of the device in terms of the plate area A and d , κ_1 , κ_2 and κ_3 .

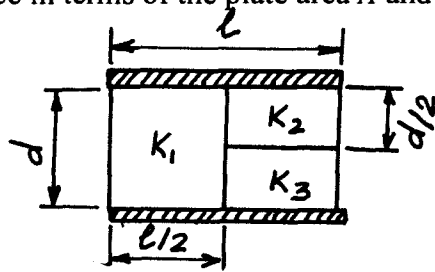


Figure 1.

2. The switch in Figure 2 is connected to point a for a long time. After the switch is thrown to point b , what are
- the frequency of oscillation of the LC circuit,
 - the maximum charge that appears on the capacitor,
 - the maximum current in the inductor
 - the total energy the circuit possesses at $t = 3$ s?

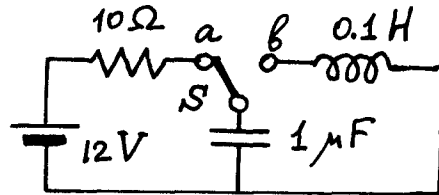


Figure 2.

3. Consider the filter circuit shown in Figure 3.
- Find the ratio of the output voltage to the input voltage
 - What value does this ratio approach as the frequency decreases toward zero? What value does this ratio approach as the frequency increases without limit?
 - At what frequency is the ratio equal to one half?

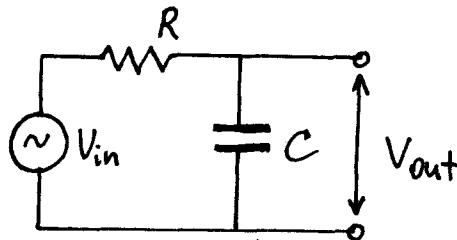


Figure 3.

4. Answer the following questions:
- If the frequency is doubled in a series RLC circuit, what happens to the resistance, the inductive reactance, and the capacitive reactance?
 - If the resistance of the wires in an LC circuit were not zero, would the oscillations persist? Explain.
 - Embodied in Kirchoff's rules are two conservation laws. What are they?
 - Two lightbulbs operate from 120 V. One has a power of 25 W and the other 100 W. Which bulb has higher resistance? Which bulb carries more current?
5. An electric current is given by the expression $I(t) = 100 \sin(120\pi t)$, where I is in amperes and t is in seconds. What is the total charge carried by the current from $t = 0$ to $t = (1/240)$ s?

Formulae

$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$\tan \varphi = \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$U_L = \frac{1}{2} LI^2$$

$$U_C = \frac{1}{2} \frac{Q^2}{C}$$

$$C = \kappa \frac{\epsilon_0 A}{d}$$

$$R = \rho \frac{l}{A}$$

$$L = \frac{N \Phi_B}{I}$$

$$C_{eq} = C_1 + C_2 + \dots$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

$$\rho = 2aq$$

$$\vec{\sigma} = \vec{\rho} \times \vec{E}$$

$$I = nq v_d A$$

$$\vec{J} = \sigma \vec{E}$$

$$\rho = \rho_0 (1 + \alpha (T - T_0))$$

$$R_{eq} = R_1 + R_2 + \dots$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$L = \mu_0 \frac{N^2 A}{l}$$

$$M_{12} = \frac{N_2 \Phi_{12}}{I_1}$$